

# Assignment 1 | FPGA Lab

Akhil Kumar Donka

January 2022

## 1 Question

Write the Product of Sum form of function  $G(U,V,W)$  for the following truth table representation of F

U	V	W	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

## 2 Solution

### 2.1 KMAP Implementation

Given truth table can be minimized using a KMap (Figure 1). Using implicants in figure, POS Terms obtained are :  $(U + \overline{W}), (V + \overline{W}), (\overline{U} + \overline{V} + W)$

		$VW$			
		00	01	11	10
$U$	0	1	0	0	1
	1	1	0	1	0

Figure 1: POS for G

## 2.2 Minimized POS Expression

$$G = (U + \overline{W}).(V + \overline{W}).(\overline{U} + \overline{V} + W)$$

## 2.3 NAND Logic Implementation

To implement it using NAND Logic, we first convert it into SOP form, which gives :

$$\begin{aligned} & \overline{V}.\overline{W} + \overline{U}.\overline{W} + U.V.W \\ & (\overline{V} + \overline{U}).\overline{W} + U.V.W \\ & \overline{V}.\overline{U}.\overline{W} + U.V.W \end{aligned}$$

The last expression can be implemented using only NAND Gates.

